









In the Name of God

# **Digital Circuit Design**








## **Chapter 7:**

# **Memory and Programmable Logic**

## ✓ Memories

- ❖ A device to which binary information is transferred for storage and from which information is retrieved when needed for processing 
- ❖ When data processing takes place, information from memory is transferred to selected registers in the processing unit and then, the final results are transferred back in memory 
- ❖  Write operation: The process of storing new information into memory 
- ❖ Read operation: The process of transferring the stored information out of memory 
- ❖ **Types of memories:** 
  - ✓ Random-Access Memory (RAM): Perform both write and read operations 
  - ✓ Read-Only Memory (ROM): Perform only the read operation 


## ✓ Random-Access Memory (RAM)

- ❖ A collection of storage cells, together with associated circuits needed to transfer information into and out of a device 
- ❖ The information can be selectively retrieved from any of its internal location 
- ❖ The times it takes to transfer data to or from any desired random location is always the same 
- ❖ A memory unit stores binary information in group of bits called word 
- ❖ A group of 8 bits is called a byte 
- ❖ Most computer memories use words that are multiples of 8 bits in length 
- ❖ The capacity of a memory unit is usually stated as the total number of bytes that the unit can store 



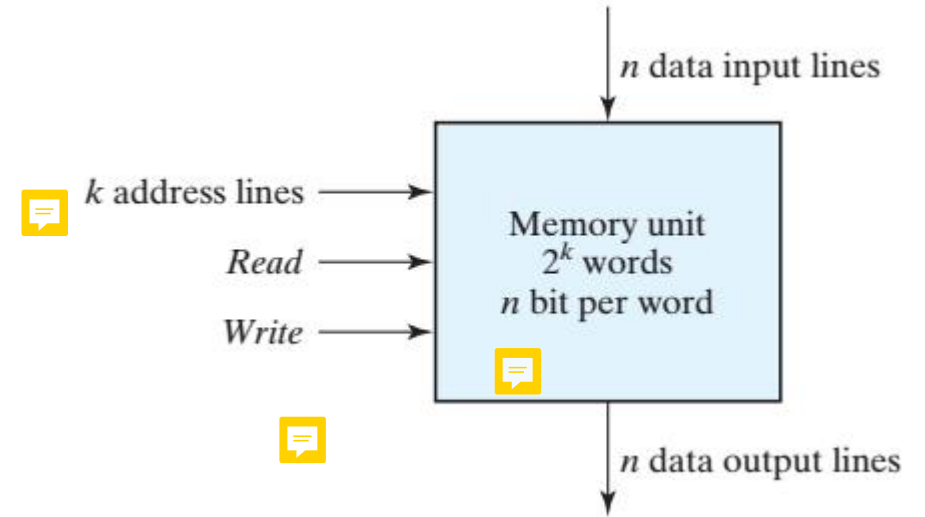
## ✓ Random-Access Memory (RAM)

- ❖ The memory unit is specified by the number of words it contains and the number of bits in each word
- ❖ Each word in memory is assigned an identification number, called address
- ❖ An internal decoder accepts this address and opens the paths needed to select the word specified
- ❖ Number of words (or bytes) in memory can be referred with one of the letters K (equals to  $2^{10}$ ), M (equals to  $2^{20}$ ), G (equals to  $2^{30}$ )
  - ✓ *1K×16 memory has 10 bits in the address and 16 bits in each word*
  - ✓ *64K×10 memory has 16 bits in the address and 10 bits in each word*




## ✓ Random-Access Memory (RAM)

### ❖ Write Operation




- ✓ Apply the binary address of the desired word to the address lines
- ✓ Apply the data bits that must be stored in memory to the data input lines 
- ✓ Activate the write input

### ❖ Read Operation

- ✓ Apply the binary address of the desired word to the address lines 
- ✓ Activate the read input

- ❖ Most ICs provide two other control inputs:  
one input selects the unit (Chip Select) and  
the other determines the operation


*Control Inputs to Memory Chip*

 Memory Enable	 Read/Write	Memory Operation
 0	X	None
1	0	Write to selected word
1	1	Read from selected word

# ✓ Random-Access Memory (RAM)
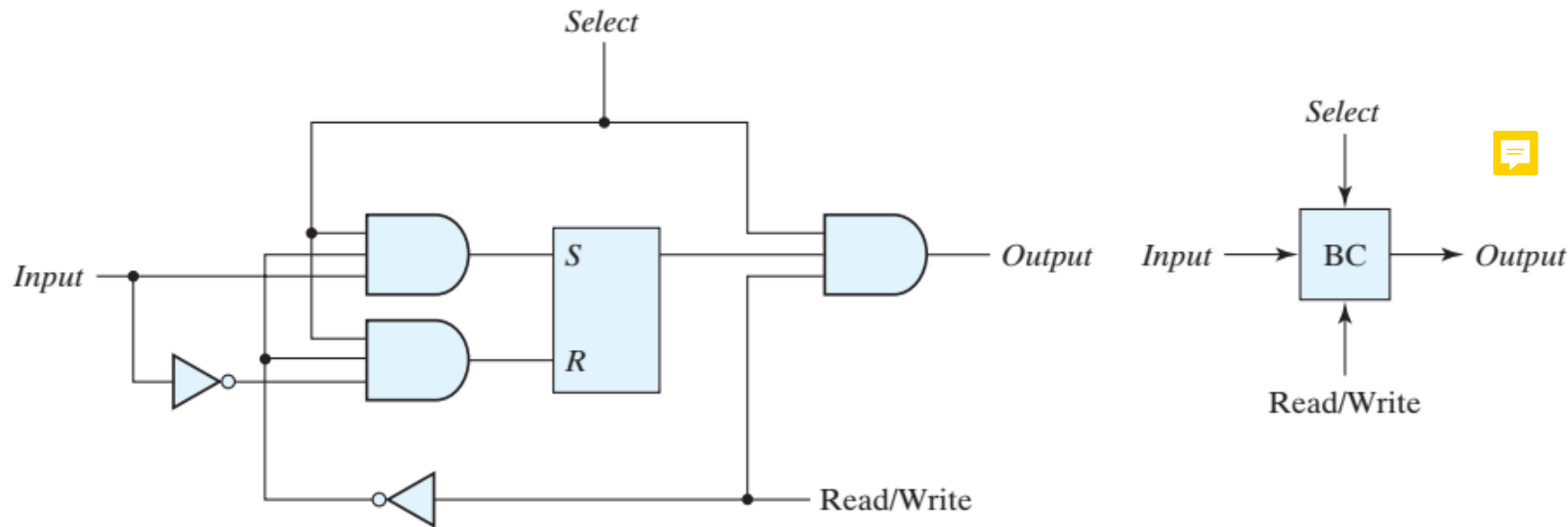
## ❖ Internal construction

✓ A binary storage cell is the basic building block of a memory unit 



✓ The binary cell (BC) stores one bit in its internal latch 


✓ The select input enables the cell for reading or writing

✓ A “1” in the read/write input **provides** the read **operation** and a “0” provides the write operation  
فرام کردن      عملیات

# ✓ Random-Access Memory (RAM)

## ❖ Internal construction

✓  $4 \times 4$  RAM

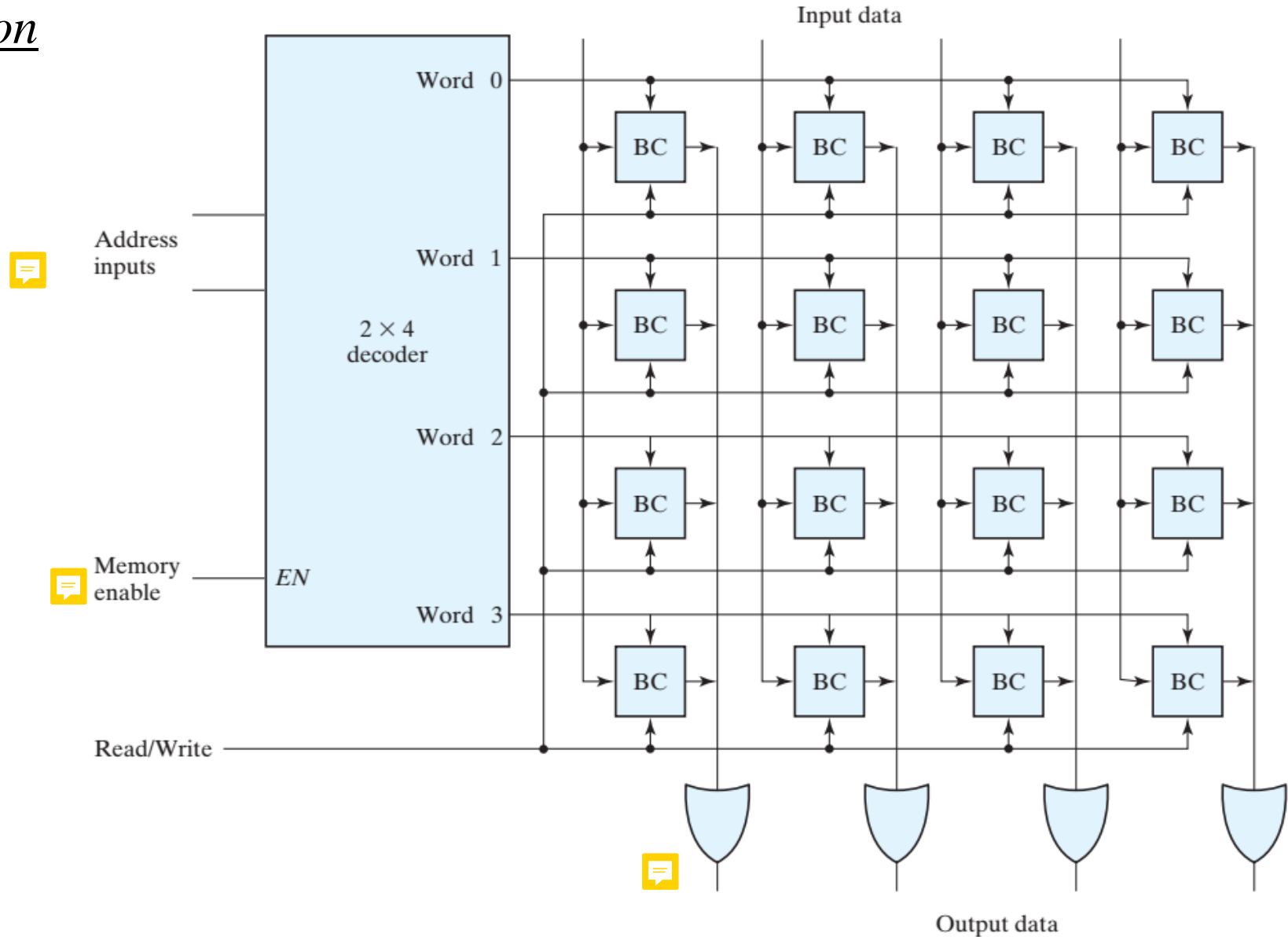


# ✓ Random-Access Memory (RAM)

## ➤ Types of RAM

✓ SRAM: Consists of internal latches that stores the binary information 

✓ DRAM: Stores the binary information in the form of electric charges on capacitors provided inside the chip by MOS transistors 

❖ DRAM offers reduced power and larger storage capacity, while SRAM is easier to use 


❖ In a Sequential-Access Memory (SAM), the information is not immediately accessible (a magnetic tape) and the time it takes to access a word depends on the position of the word 

❖ In RAMs, the stored information are removed when power is turned off 



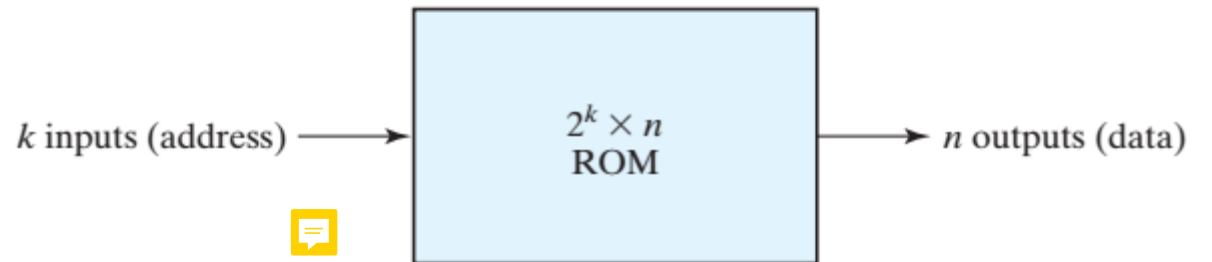
## ✓ Read-Only Memory (ROM)

- ❖ A memory device in which permanent binary information is stored
- ❖ Performs only read operation
- ❖ The binary information stays within the unit even when power is turned off and on again
- ❖ ROM does not have data inputs



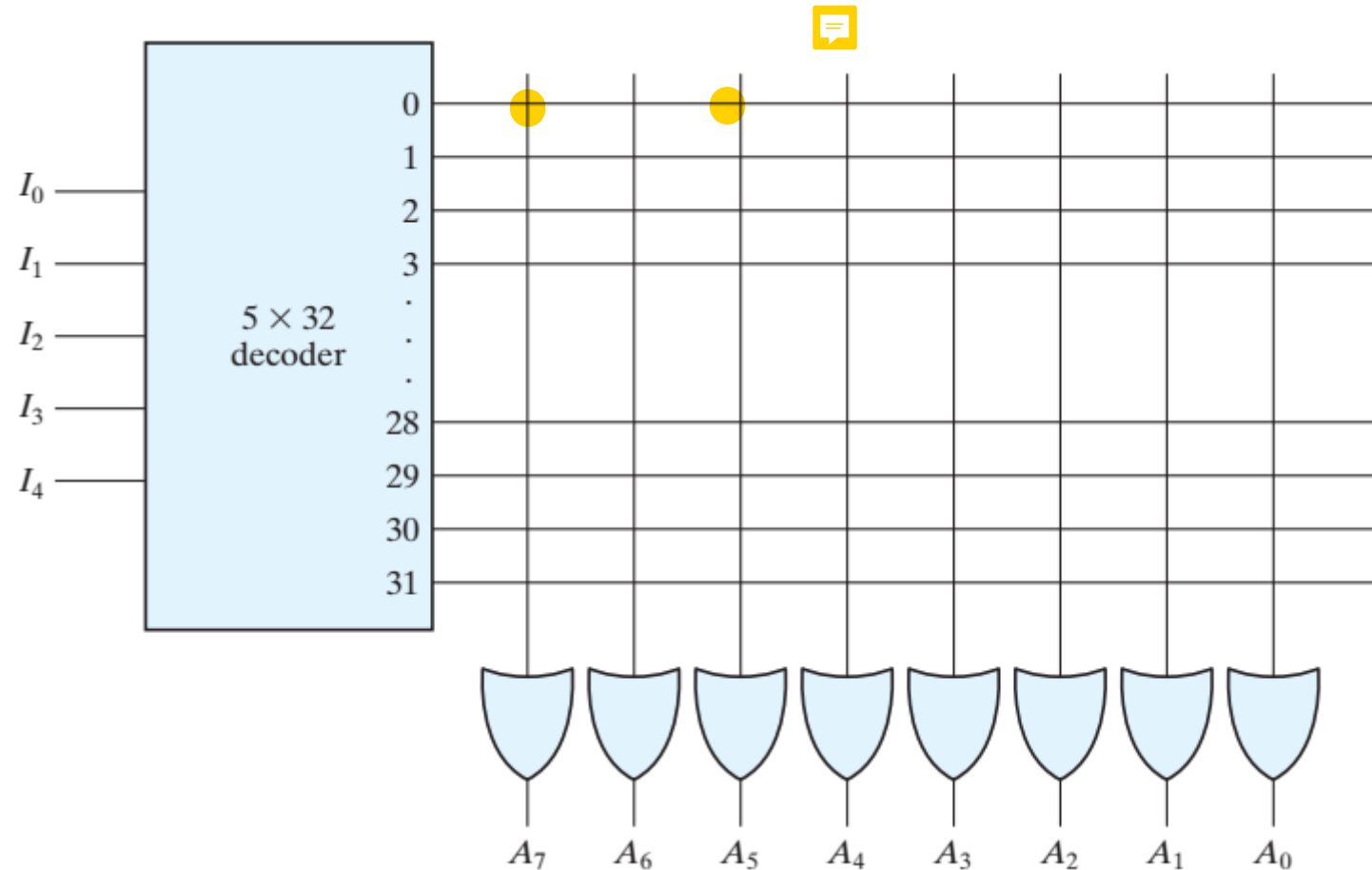
## ✓ Read-Only Memory (ROM)

- ❖ A  $32 \times 8$  ROM
- ❖ The 32 outputs of the decoder are connected to each of the eight OR
- ❖ Each OR gate must be considered as having 32 inputs
- ❖ The ROM contains  $32 \times 8 = 256$  internal connections
- ❖ In general, a  $2^k \times n$  ROM will have an internal  $k \times 2^k$  decoder and  $n$  OR gates


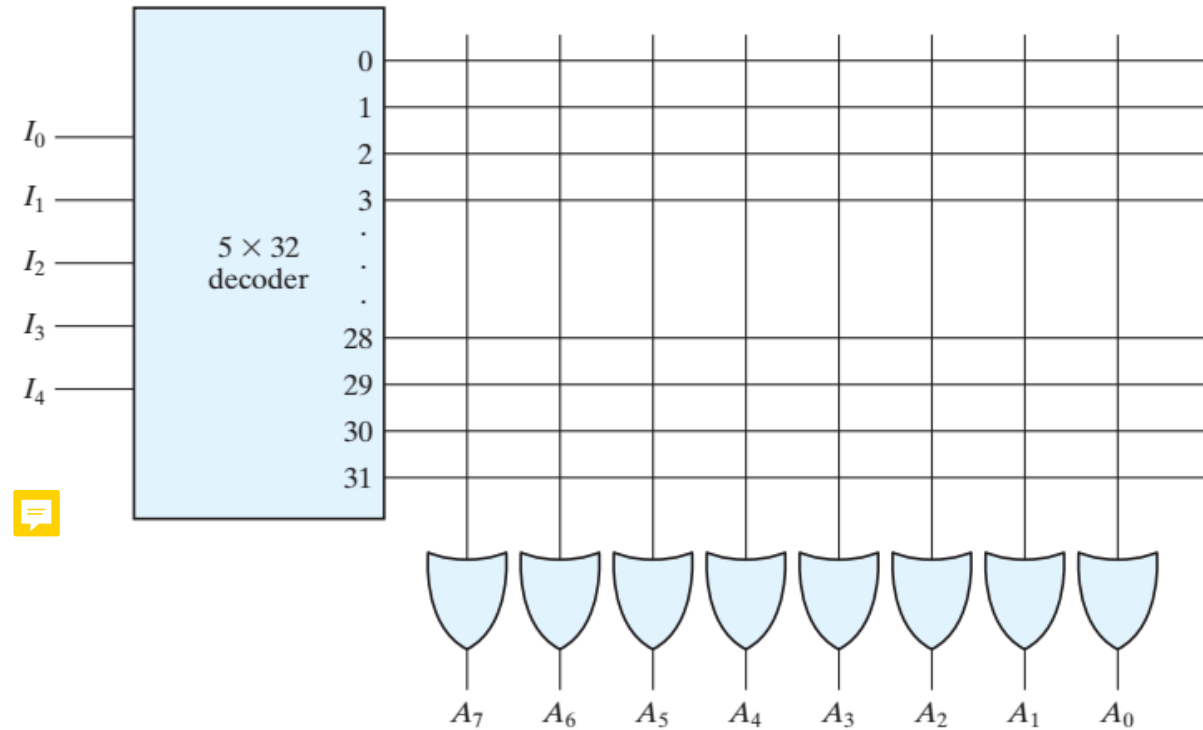
## ✓ Read-Only Memory (ROM)

- ❖ The 256 intersections are programmable
- ❖ A programmable connection between two lines is logically equivalent to a switch
  - ✓ Closed: meaning that two lines are connected
  - ✓ Opened: meaning that two lines are disconnected
- ❖ One of the simplest technology employs a fuse
  - ✓ Normally connects two points
  - ✓ Is opened (blown) by the application of a high-voltage pulse into the fuse




## ✓ Read-Only Memory (ROM)

- ❖ The internal binary storage of a ROM is specified by truth table
- ❖ The hardware procedure that programs the ROM, blows fuse links in accordance with a given truth table

ROM Truth Table (Partial)

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮						⋮				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1
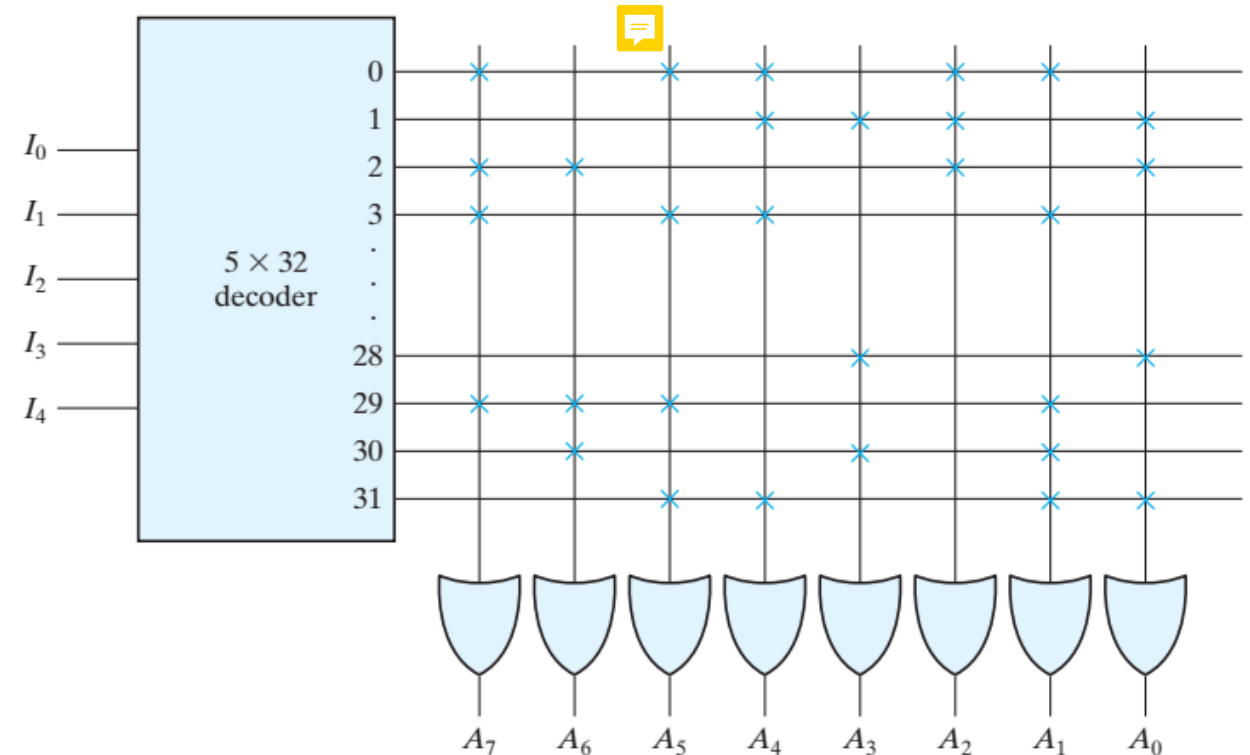
$$A_7(I_4, I_3, I_2, I_1, I_0) = \Sigma(0, 2, 3, \dots, 29)$$



## ✓ Read-Only Memory (ROM)

➤ **Types of ROMs:** *The required paths in ROM may be programmed in four different ways* 🗨️

### ❖ Mask programming: 🗨️

- ✓ Done by the semiconductor company during the fabrication 🗨️
- ✓ This procedure is costly, thus is economical only for a large quantity of the same ROM 🗨️

### ❖ PROM (Programmable ROM): 🗨️

- ✓ Contain all the fuses intact and can be blown by the application of a high-voltage pulse 🗨️

### ❖ EPROM (Erasable PROM): 🗨️

- ✓ Can be restructured to the initial state by placing under a special ultraviolet light 🗨️

### ❖ EEPROM (Electrically Erasable PROM): 🗨️

- ✓ The previously programmed connections can be erased with an electrical signal 🗨️
- ✓ The device can be erased without removing it from its socket 🗨️