

به نام خدا

طراحی سیستم های دیجیتال ۱

فصل چهارم

مدارهای منطقی ترکیبی

Combinational Logic Circuits

✓ مدارهای منطقی ترکیبی

❖ مدارهای منطقی:

✓ ترکیبی: خروجی در هر لحظه به ورودی در همان لحظه وابسته است.

✓ ترتیبی: خروجی در هر لحظه به ورودی در همان لحظه و به مقادیر قبلی خروجی وابسته است.

❖ مهمترین مدارهای منطقی ترکیبی:

Adders ✓

Subtractors ✓

Decoders ✓

Encoder ✓


Multiplexer ✓

✓ مدارهای منطقی ترکیبی

❖ روند آنالیز (Analysis Procedure):

✓ در آنالیز مدار ترکیبی پیاده سازی شده را داریم و باید از روی آن ضابطه تابع، جدول صحت و تابع ساده شده را بدست بیاوریم.

❖ مثال:

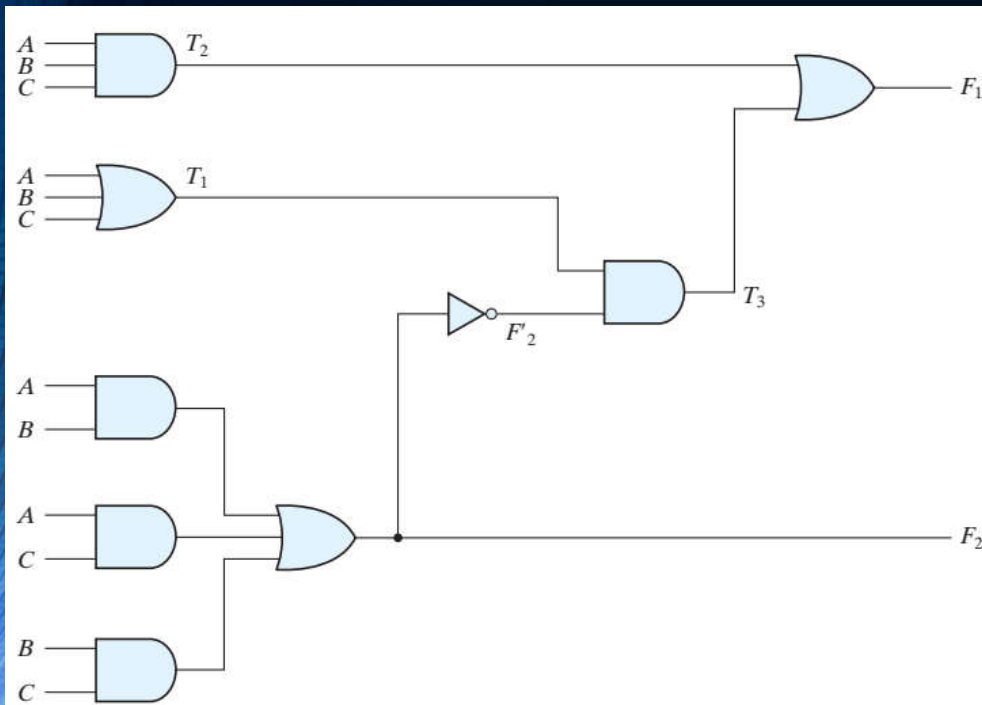

$$F_2 = AB + AC + BC$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

I

A	B	C	F_2	F'_2	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

ABC

✓ مدارهای منطقی ترکیبی

❖ روند طراحی (Design Procedure):

✓ در طراحی صورت مسئله را داریم و باید از روی آن باید ضابطه تابع و درنهایت پیاده سازی را انجام داد.

✓ صورت مسئله ← جدول صحت ← استخراج تابع از روی جدول صحت ← ساده سازی تابع ← پیاده سازی

❖ مثالی از کد گردانی (Code Conversion):


طراحی یک مدار برای تبدیل کد BCD به
Excess-3

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

✓ مدارهای منطقی ترکیبی

❖ مثالی از کد گردانی (Code Conversion):

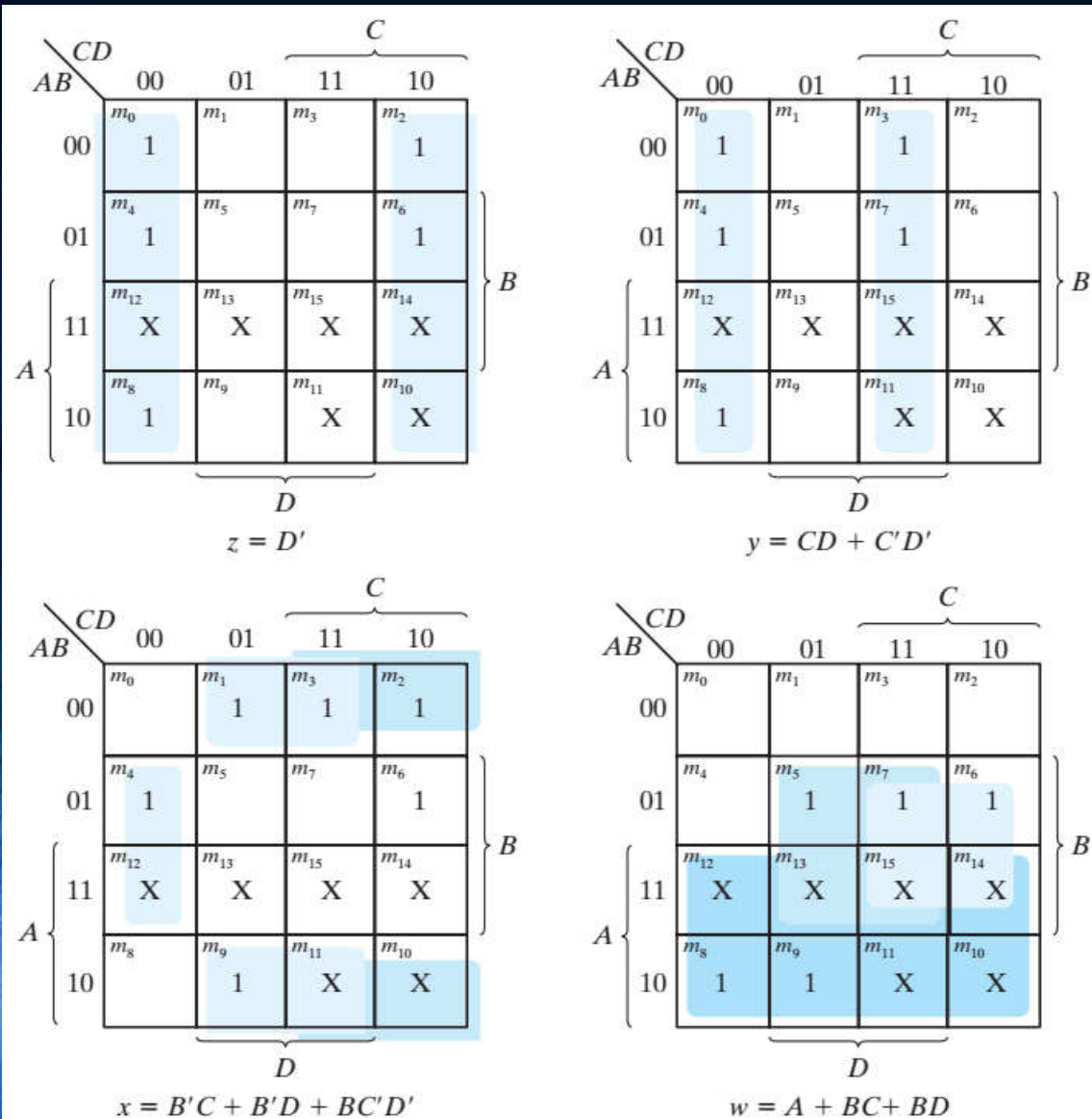طراحی یک مدار برای تبدیل کد BCD به
Excess-3




✓ مدارهای منطقی ترکیبی

❖ مثالی از کد گردانی :

طراحی یک مدار برای تبدیل


کد BCD به Excess-3

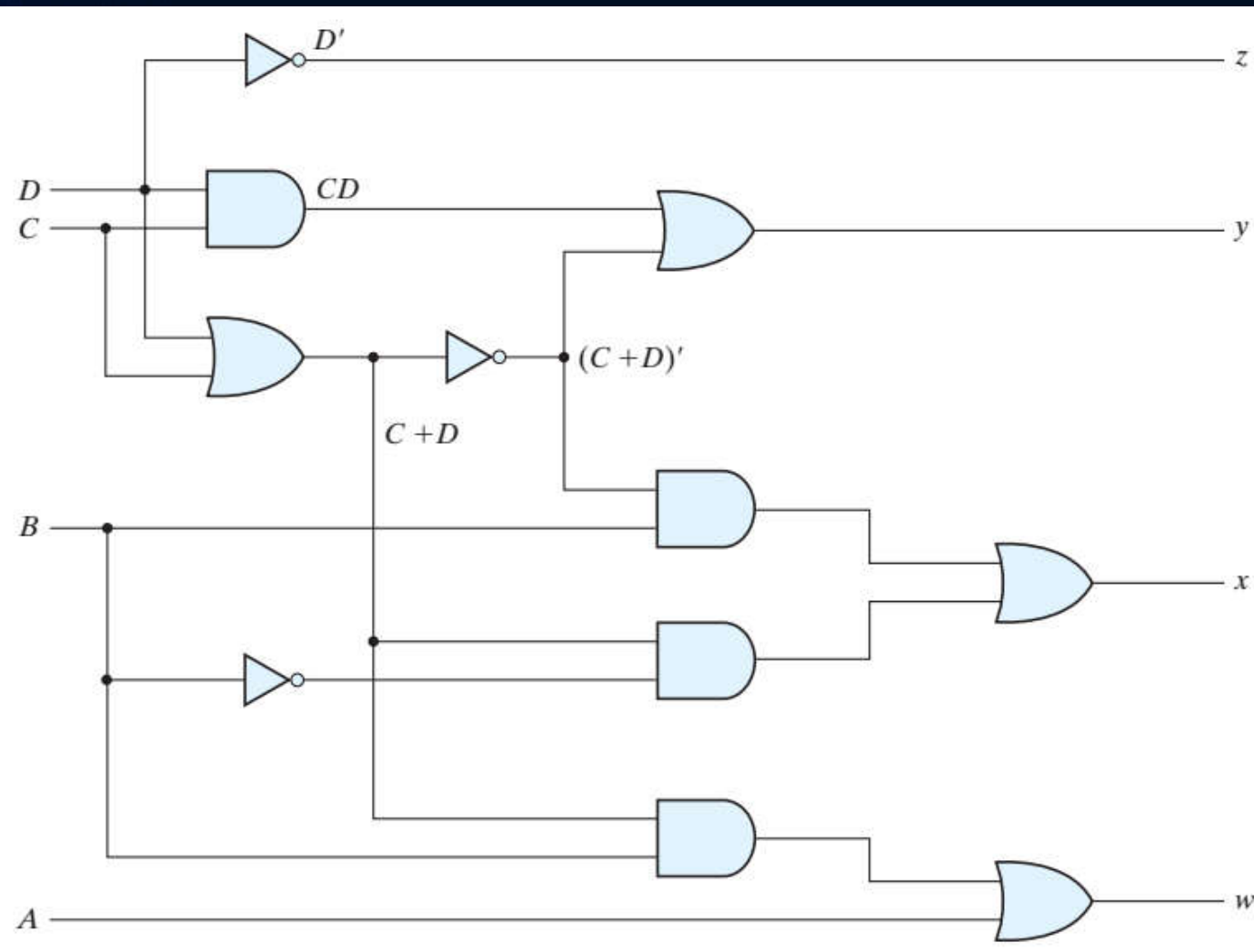

✓ مدارهای منطقی ترکیبی


❖ مثال: مداری طراحی کنید که اگر در آن $C=0$ شد، چهار ورودی A نظیر به نظیر به چهار خروجی F منتقل

 شود. در غیراینصورت چهار ورودی B به چهار خروجی F منتقل شود.




$$F_i = \sum m(2, 3, 5, 7)$$

$$F_i = C'A_i + CB_i$$

 


C	A_i	B_i	F_i
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


✓ Decoders

 - ❖ An n -to- 2^n decoder is a multiple-output combinational logic with n input and 2^n output
- ❖ For each possible input condition, one and only one output will be at logic 1




✓ Decoders

 - 2-to-4 decoder
- ❖ We can consider the n -to- 2^n decoder as simply a **minterm generator**
- ❖ An input combination of $BA=00$ selects the m_0 output line, $BA=01$ selects the m_1 and so on.




$$\begin{aligned}m_0 &= \bar{B}\bar{A} \\m_1 &= \bar{B}A \\m_2 &= B\bar{A} \\m_3 &= BA\end{aligned}$$

✓ Decoders

 

Using only NAND gates

 


Using only NAND gates
with no inverters

- ❖ An output of 0 indicates the presence of the corresponding minterms
- ❖ In this case, the outputs are said to be “active low”



✓ Decoders

3-to-8 Decoder (parallel-type)

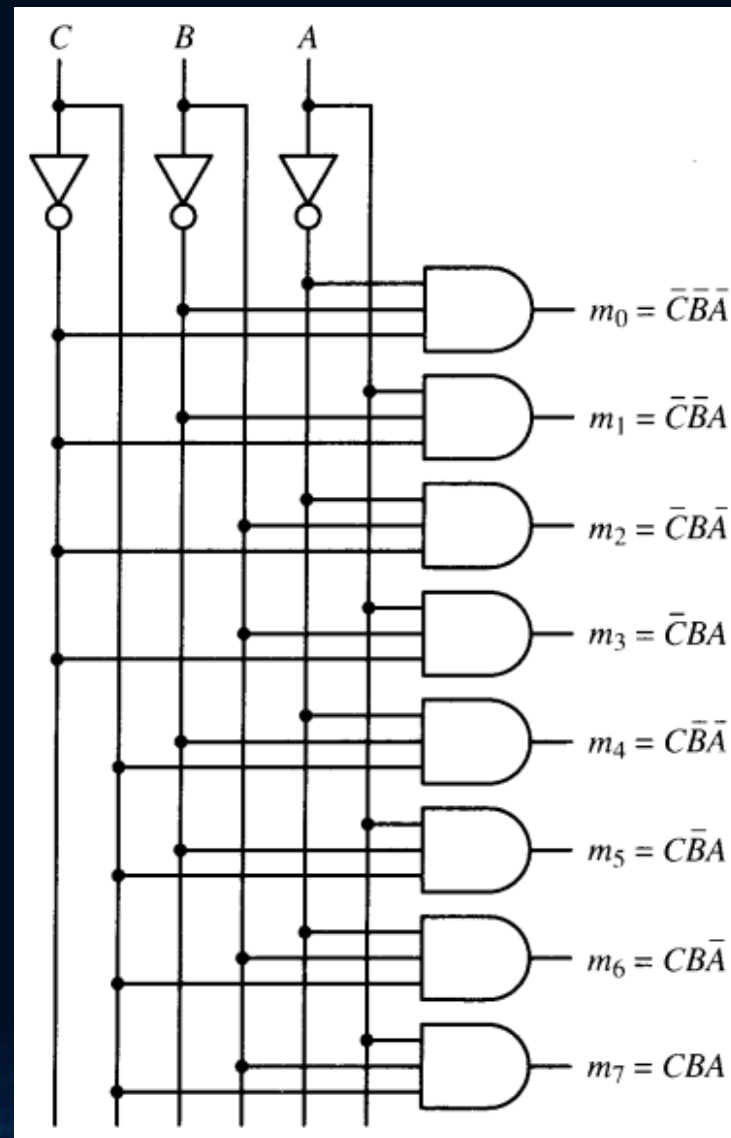

✓ Decoders

  - ❖ There is only a single level of logic
- ❖ One n input AND gate is required for each of the 2^n output lines
- ❖ A problem is occurred as n becomes large because of limitation of the fan-in
- ❖ So, tree decoder has been proposed





✓ Decoders

❖ Tree Decoder: employs multilevel logic with only two-input AND gates, independent of the number of input lines

❖ Dual Tree Decoder:

✓ n input are divided into j and k groups

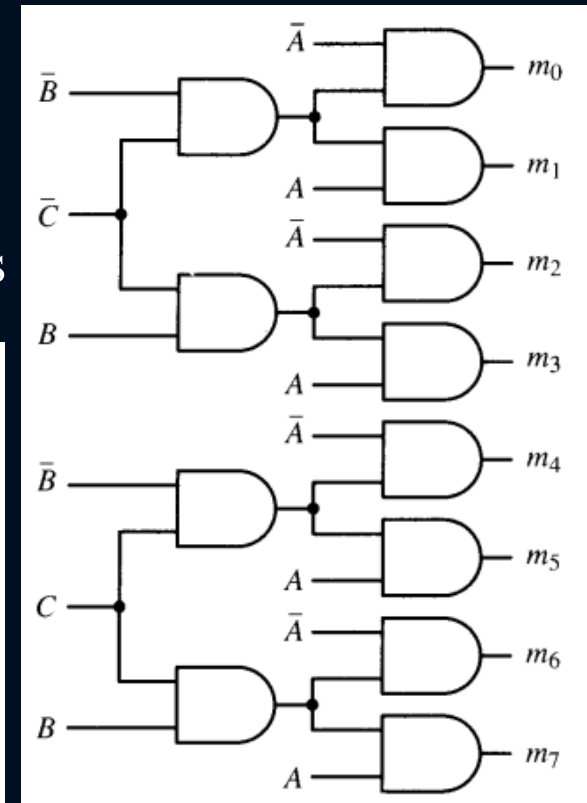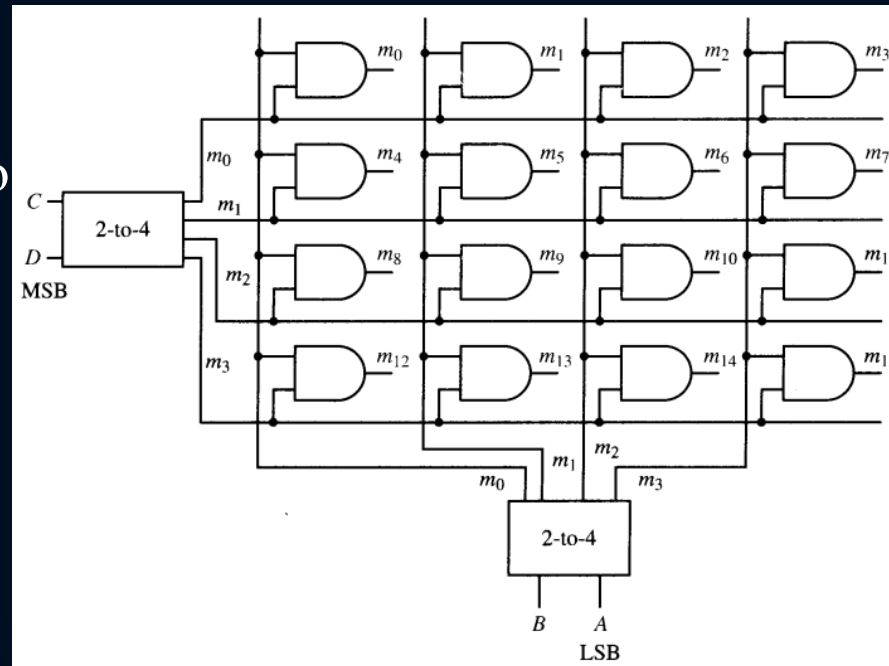✓ Two smaller decoders j-to- 2^j and k-to- 2^k are used



✓ Two-input AND gates are used to combine these signals to form the 2^n output lines

✓ Decoders

❖ Implementing logic function

- ✓ Decoders output signals in complement form are suitable for further processing using NAND logic

$$f(A, B, \dots, Z) = m_i + m_j + \dots + m_k \quad \longrightarrow \quad f(A, B, \dots, Z) = \overline{\bar{m}_i \cdot \bar{m}_j \cdot \dots \cdot \bar{m}_k}$$

- ✓ This function can be implemented using a single k-input NAND gate and a decoder with active-low outputs

- ✓ This is equal to implement a function with its maxterm

$$M_i = \bar{m}_i$$

$$f(A, B, \dots, Z) = M_i \cdot M_j \cdot \dots \cdot M_k$$

→ Using a decoder with active low outputs and an AND gate

✓ Decoders

➤ Example: Implement the following function



$$\begin{aligned} f(Q, X, P) &= \sum m(0, 1, 4, 6, 7) \\ &= \prod M(2, 3, 5) \end{aligned}$$

❖ Use a decoder (with active high outputs) with an OR gate

$$f(Q, X, P) = m_0 + m_1 + m_4 + m_6 + m_7$$

❖ Use a decoder (with active low outputs) with an NAND gate
  
$$f(Q, X, P) = \overline{\bar{m}_0 \cdot \bar{m}_1 \cdot \bar{m}_4 \cdot \bar{m}_6 \cdot \bar{m}_7}$$



✓ Decoders

❖ Example:



$$\begin{aligned} f(Q, X, P) &= \sum m(0, 1, 4, 6, 7) \\ &= \prod M(2, 3, 5) \end{aligned}$$

- ❖ Use a decoder (with active high outputs) with an NOR gate

$$f(Q, X, P) = \overline{m_2 + m_3 + m_5}$$

- ❖ Use a decoder (with active low outputs) with an AND gate

  
$$f(Q, X, P) = \bar{m}_2 \cdot \bar{m}_3 \cdot \bar{m}_5$$



✓ Decoders

➤ Enable Control Input


- ❖ Enable Inputs can be used to either enable or disable the designated functions to be performed
- ❖ The decoding function of a decoder is disabled by forcing all its outputs to the inactive state
- ❖ In general, we have $y_k = m_k E$
When $E=0$, all outputs are forced to 0, whereas for $E=1$, y_k is equal to m_k
- ❖ A common use of the enable function of a decoder is to extend the decoding capability to implement larger decoder by cascading smaller decoders

 

✓ Decoders



➤ Use of 2-to-4 decoder to realize 3-to-8 decoder

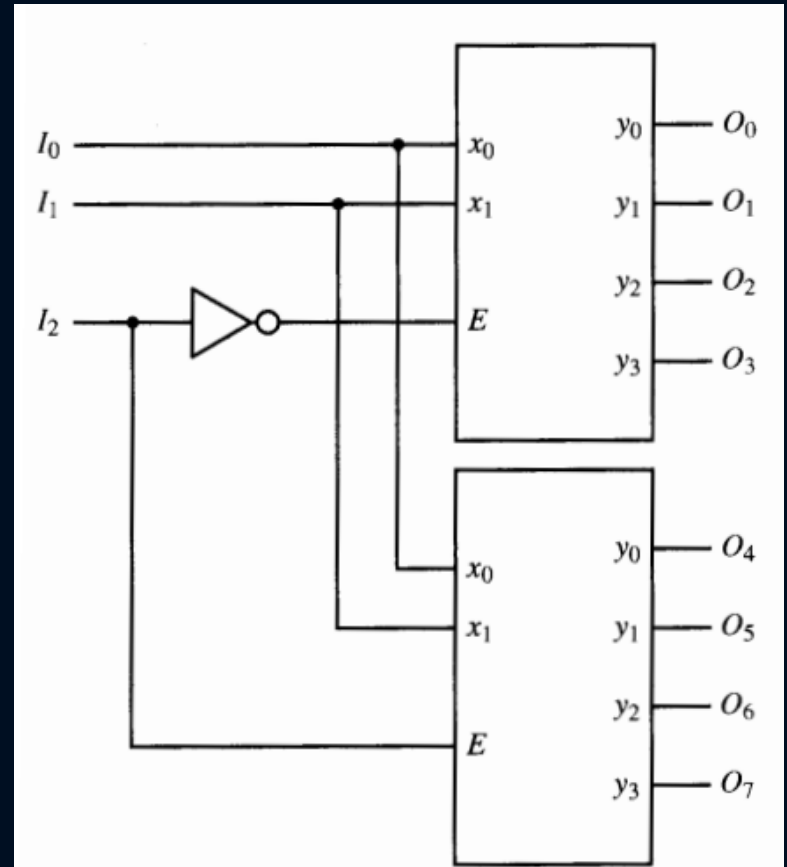- ❖ Input $I_2 = 0$ enables the top decoder
- ❖ Thus, generates input codes $I_2 I_1 I_0$ equal to 000, 001, 010, 011 (codes 0 through 3)
- ❖ Input $I_2 = 1$ enables the bottom decoder
- ❖ Thus, generates input codes $I_2 I_1 I_0$ equal to 100, 101, 110, 111 (codes 4 through 7)




✓ Decoders

 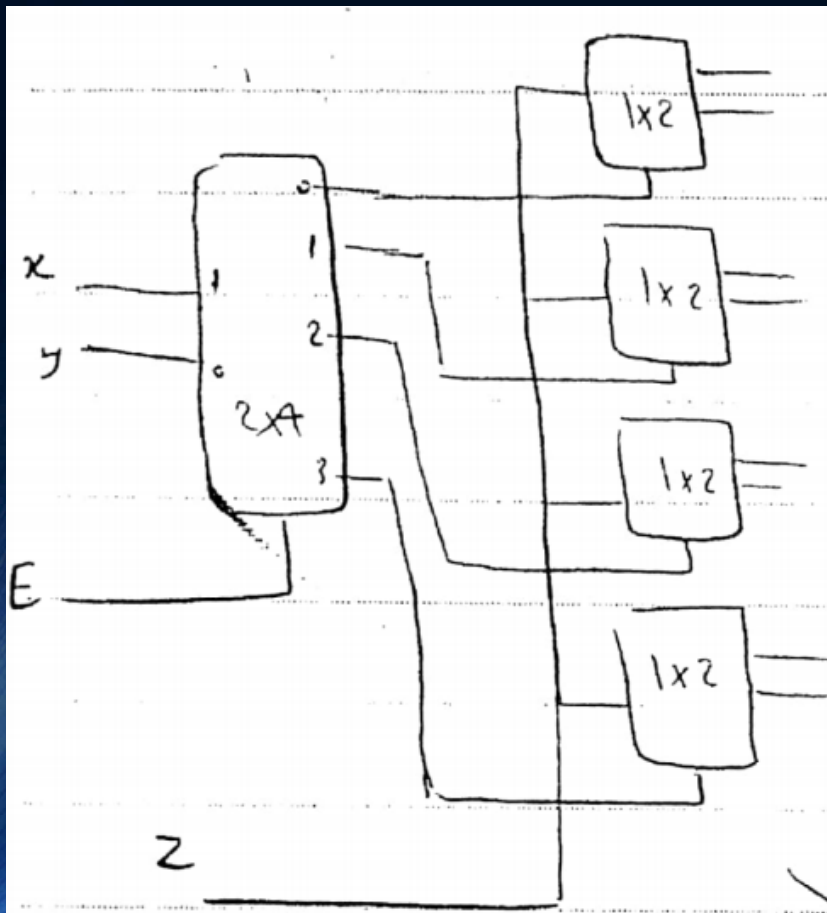- Use of 2-to-4 and 1-to-2 decoder to realize 3-to-8 decoder



✓ Decoders

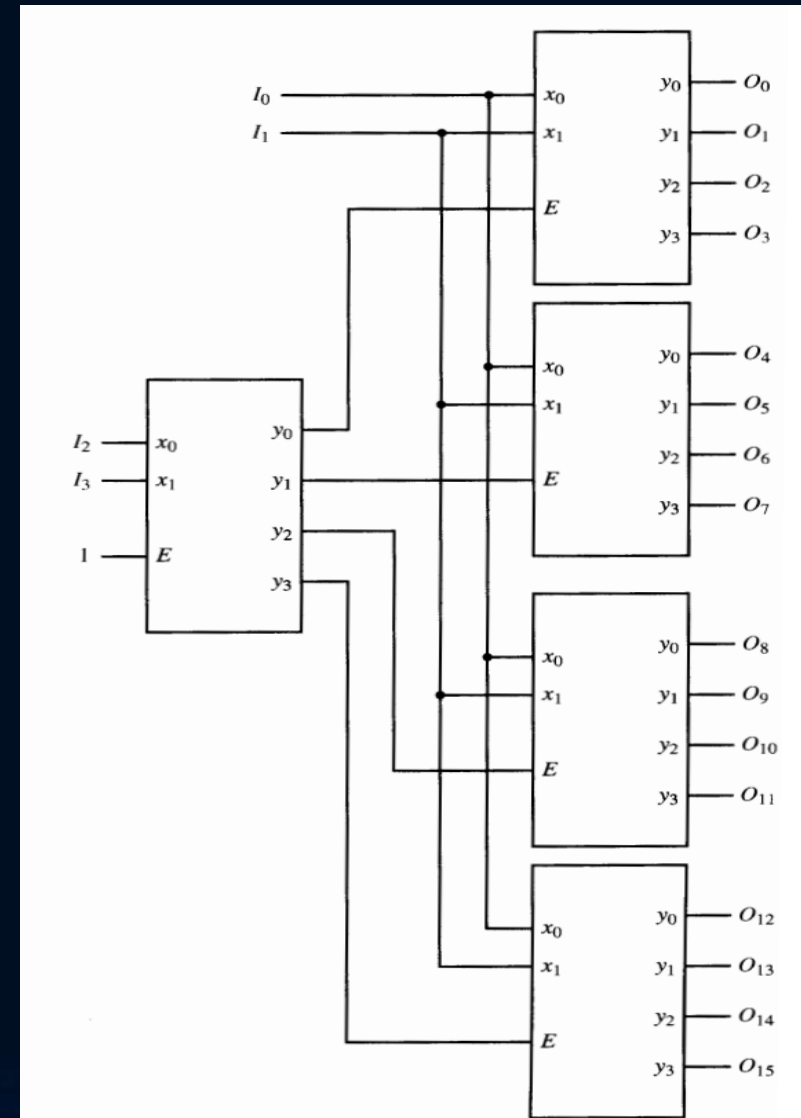- ❖ Use of 2-to-4 decoder to realize 4-to-16 decoder
- ❖ Two common standard MSI decoders are 74138 (3-to-8 decoder) and 74154 (4-to-16 decoder)
- ❖ *Decoder Applications:*
 - ✓ Address Decoding (Computer Memories)
 - ✓ Minterm Generation
 - ✓ Code Converter (BCD to Decimal, ...)
 - ✓ Display Decoders (7-Segment)





✓ Encoders

❖ An Encoder is the opposite of a decoder which has 2^n input lines and n output lines

➤ Encoder Circuit Structure

▪ *Encoders with Mutually Exclusive Inputs*

  - ✓ One and only one of the input lines is active
- ✓ Two or more input lines are never simultaneously active
- ✓ The input combinations that never occur may be used as don't-care
- ✓ The output functions yield the binary value of the input variable's subscript



X_3	X_2	X_1	X_0	A_1	A_0
0	0	0	0	<i>d</i>	<i>d</i>
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	<i>d</i>	<i>d</i>
0	1	0	0	1	0
0	1	0	1	<i>d</i>	<i>d</i>
0	1	1	0	<i>d</i>	<i>d</i>
0	1	1	1	<i>d</i>	<i>d</i>
1	0	0	0	1	1
1	0	0	1	<i>d</i>	<i>d</i>
1	0	1	0	<i>d</i>	<i>d</i>
1	0	1	1	<i>d</i>	<i>d</i>
1	1	0	0	<i>d</i>	<i>d</i>
1	1	0	1	<i>d</i>	<i>d</i>
1	1	1	0	<i>d</i>	<i>d</i>
1	1	1	1	<i>d</i>	<i>d</i>

$$A_1 = X_3 + X_2$$
$$A_0 = X_3 + X_1$$

✓ Encoders

➤ Encoder Circuit Structure

▪ *Priority Encoders*


	A_1	A_0
$X_0 \rightarrow$	0	0
$X_1 \rightarrow$	0	1
$X_2 \rightarrow$	1	0
$X_3 \rightarrow$	1	1

- ✓ Multiple input lines can be active
- ✓ Sends out the binary value of the subscript of the input line with highest priority
- ✓ The highest priority is assigned to the highest subscript
- ✓ If no input line is active, the priority encoder sends out (00)
- ✓ If a single line is active, the encoder sends out the binary value of the subscript of the active line
- ✓ If more than one input is active, the encoder sends out the binary value of the largest subscript of the active lines

✓ Encoders

➤ Encoder Circuit Structure

■ *Priority Encoders*

 


- ✓ Two additional output lines indicates that no input line is active (EO=1) and one or more inputs are active (GS=1)

Inputs				Outputs			
X_3	X_2	X_1	X_0	A_1	A_0	GS	EO
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	0
1	0	0	0	1	1	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	1	1	0
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	0

$$A_1 = X_2 + X_3$$


$$A_0 = X_3 + X_1\bar{X}_2$$
 
$$EO = \overline{GS} = \overline{X_3 + X_2 + X_1 + X_0}$$




✓ Encoders

➤ Standard MSI Encoders

 



74147

 

74148

✓ Multiplexers

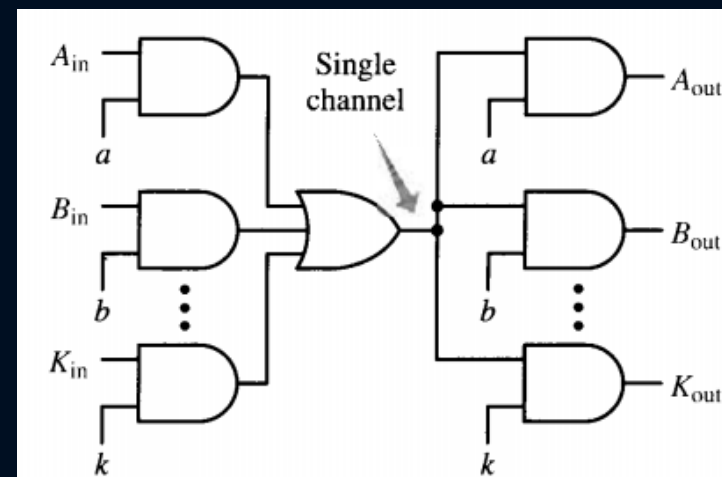
 
- ❖ *Multiplexers (Data Selectors)* is a modular device that selects one of many input lines to appear on a single output line
- ❖ A *demultiplexer* performs the inverse operation which takes a single input line and routes it to one of several output lines



✓ Multiplexers

➤ Multiplexer Circuit Structure

 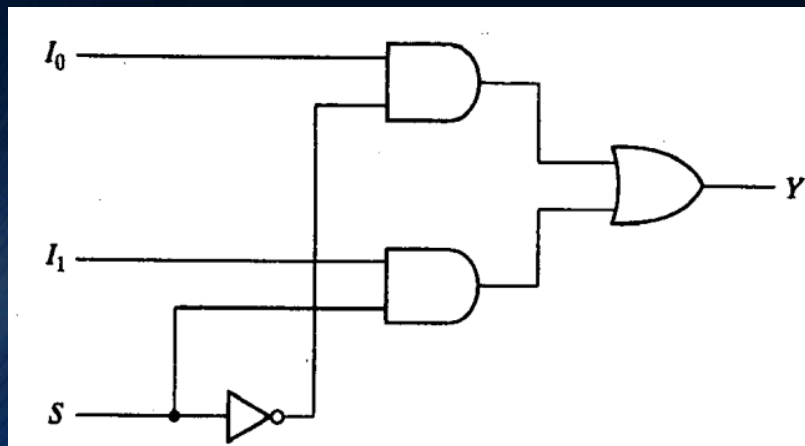
- ✓ The selection of a particular input line is controlled by a set of selection lines
- ✓ There are 2^n input lines and n selection lines
- ✓ A 2-to-1 multiplexer has two data input lines, one output line and one selection line



✓ Multiplexers

➤ Multiplexer Circuit Structure


✓ A 4-to-1 multiplexer

 

B	A	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$Y = (\bar{B}\bar{A})D_0 + (\bar{B}A)D_1 + (B\bar{A})D_2 + (BA)D_3$$

$$Y = \sum_{i=0}^3 m_i D_i$$

 


✓ m_i are the minterms of the selection code

✓ The delay of the all 2^n -to-1 multiplexers is 2, because of their SOP forms

✓ Multiplexers

➤ Multiplexer Circuit Structure


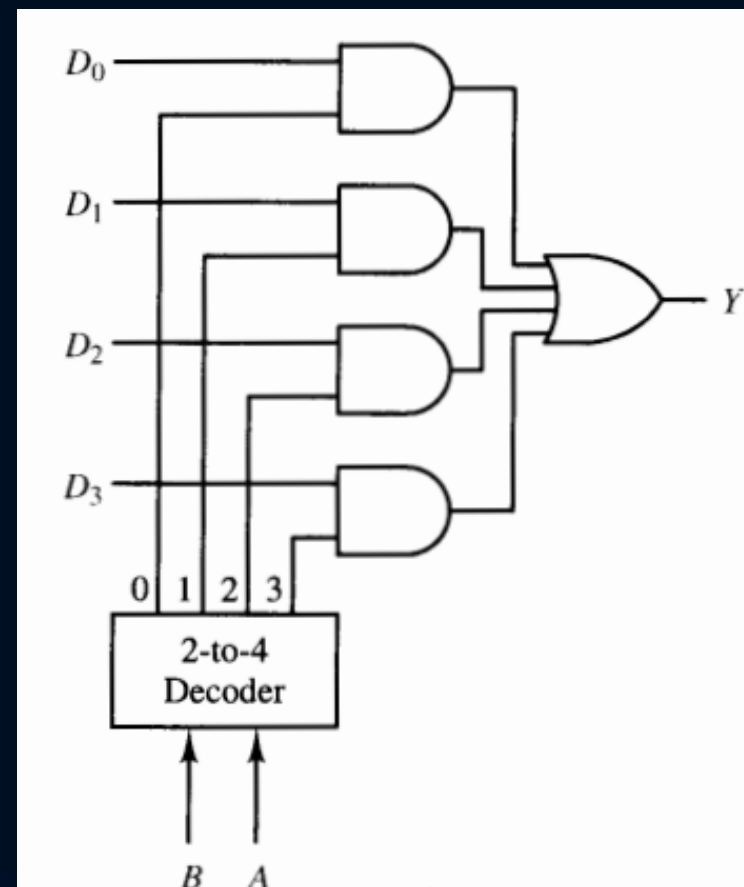
- ✓ In general, a 2^n -to-1 line multiplexer is constructed from an n -to- 2^n decoder by adding 2^n input lines to it, one to each AND gate



✓ Multiplexers

➤ Multiplexer Circuit Structure

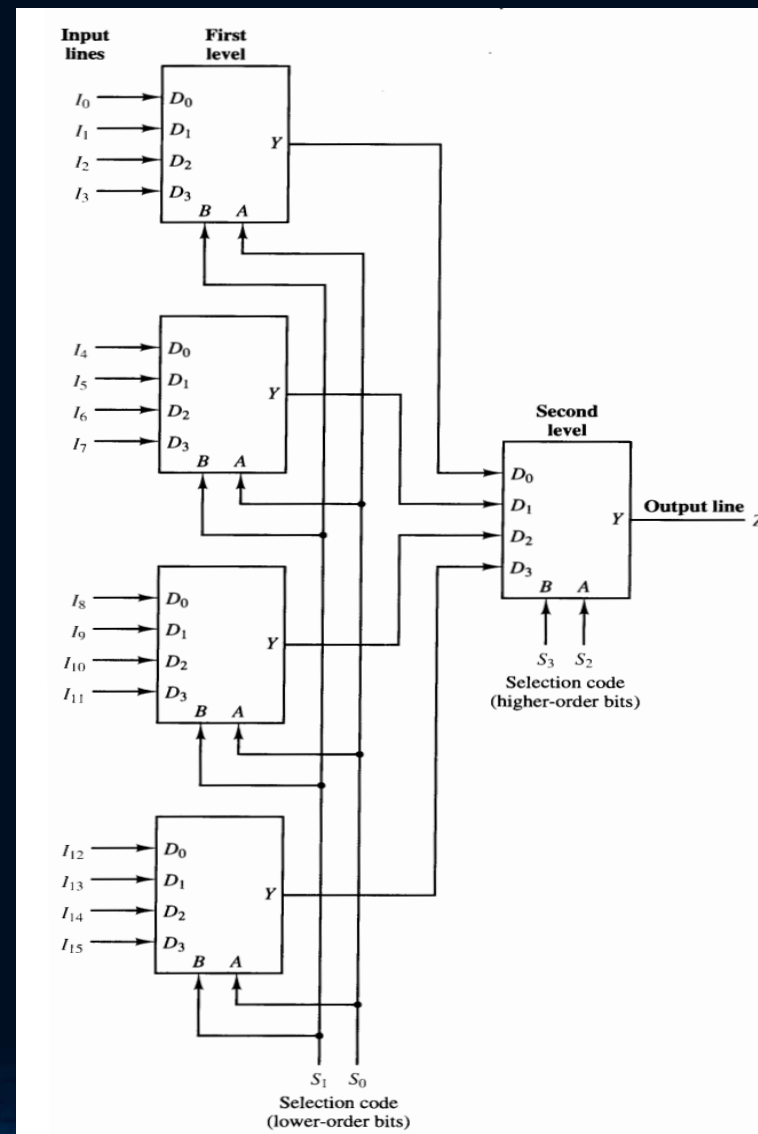 - ✓ 16-to-1 multiplexer using 4-to-1 multiplexers
- ✓ 4-to-1 multiplexer using 2-to-1 multiplexers




✓ Multiplexers

➤ Implementing logic functions

- ✓ Ex. Implement the function using 74151A (8×1 MUX)

$$f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$$

x_1	x_2	x_3	f	
0	0	0	1	$D_0 = 1$
0	0	1	0	$D_1 = 0$
0	1	0	1	$D_2 = 1$
0	1	1	1	$D_3 = 1$
1	0	0	0	$D_4 = 0$
1	0	1	1	$D_5 = 1$
1	1	0	0	$D_6 = 0$
1	1	1	0	$D_7 = 0$

 

✓ Multiplexers

➤ Implementing logic functions

✓ Ex. Implement the function using a 4×1 MUX

$$f(a,b,c) = ab + \bar{b}c$$

$$\begin{aligned} f &= abc + ab\bar{c} + a\bar{b}c + \bar{a}\bar{b}\bar{c} \\ &= \sum m(1, 5, 6, 7) \end{aligned}$$


a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$f=c \quad D_0$$

$$f=0 \quad D_1$$

$$f=c \quad D_2$$


$$f=1 \quad D_3$$

 

✓ Multiplexers

- Ex. Implement the function using a 8×1 MUX
 
$$f(X_1, X_2, X_3, X_4) = \sum m(0, 1, 2, 3, 4, 9, 13, 14, 15)$$





a	b	c	d	f	
0	0	0	0	1	$f=1$ D ₀
0	0	0	1	1	$f=1$ D ₁
0	0	1	0	1	$f=1$ D ₂
0	0	1	1	1	$f=1$ D ₃
0	1	0	0	0	$f=d$ D ₄
0	1	0	1	0	$f=0$ D ₅
0	1	1	1	0	$f=0$ D ₆
1	0	0	0	0	$f=d$ D ₇
1	0	0	1	1	$f=0$ D ₈
1	0	1	0	0	$f=0$ D ₉
1	0	1	1	0	$f=0$ D ₁₀
1	1	0	0	0	$f=d$ D ₁₁
1	1	0	1	1	$f=0$ D ₁₂
1	1	1	0	1	$f=1$ D ₁₃
1	1	1	1	1	$f=1$ D ₁₄
1	1	1	1	1	$f=1$ D ₁₅

✓ Demultiplexers

- ❖ *Demultiplexer (Data Distributor)* connects a single input line to one of n output lines
- ❖ The selection code is used to generate a minterm of s variables
- ❖ That minterm gates the input data to the proper output terminal
- ❖ The enable signal (E) controls the operation of the circuit


$$Y_i = (m_i D) E$$

  

✓ Magnitude Comparator

- ❖ Perform a magnitude comparison of two binary numbers A and B
- ❖ The outcome of a comparison is specified by three binary variables that indicate whether $A > B$, $A < B$ or $A = B$
- ❖ So, the comparator will generate three output signal as:
 
$$\begin{array}{ll} f_1 = 1, & \text{if } A < B \\ f_2 = 1, & \text{if } A = B \\ f_3 = 1, & \text{if } A > B \end{array}$$



✓ Magnitude Comparator

❖ Design:

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

➤ $f_{A=B}$:

$$x_i = A_i \oplus B_i = A_i B_i + \overline{A_i} \overline{B_i}, i = 0, 1, 2, 3, \dots$$

$$f_{A=B} = x_0 \cdot x_1 \cdot x_2 \cdot x_3$$

➤ $f_{A>B}$:

$$A_3 > B_3 \text{ or}$$

$$A_3 = B_3 \text{ and } A_2 > B_2 \text{ or}$$

$$A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 > B_1 \text{ or}$$

$$A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 > B_0$$

$$f_{A>B} = A_3 \overline{B_3} + x_3 A_2 \overline{B_2} + x_3 x_2 A_1 \overline{B_1} + x_3 x_2 x_1 A_0 \overline{B_0}$$

3-level

➤ $f_{A<B}$:

$$f_{A<B} = \overline{A_3} B_3 + x_3 \overline{A_2} B_2 + x_3 x_2 \overline{A_1} B_1 + x_3 x_2 x_1 \overline{A_0} B_0$$


3-level

$$f_{A<B} = f_{A>B} \oplus f_{A=B}$$

4-level

✓ مثال

 ❖ مداری طراحی کنید که دارای دو ورودی BCD بوده و عدد بزرگتر را در خروجی نشان دهد.



❖ ۳ مرحله تاخیر برای مقایسه کننده و ۲ مرحله تاخیر برای مالتی پلکسر داریم که در مجموع ۵ مرحله تاخیر خواهیم داشت.